

SINGLE-STAGE RC COUPLED CE AMPLIFIER

Aim:

- i. To design a single stage RC coupled CE amplifier for the given specifications.
- ii. To plot its frequency response.

Designing equations:

Q: Design a single stage RC coupled amplifier using a BJT in CE configuration to provide a gain of 100, lower cutoff frequency 55Hz and an upper cutoff frequency of 55 KHz. Use BC547 for which $\beta=200$, $h_{fe}=50$, $h_{ie}=1.5K\Omega$ and $V_{BE(Active)}=0.65V$. The biasing conditions are as follows.

$V_{CC}=12V$, $I_C=1mA$, $V_{CE}=6V$ and Stability factor is $S=10$. Use $R_C=4.7K\Omega$

Design:

Use $I_C = \beta I_B$

$$\Rightarrow I_B = 5 \mu A$$

Apply KVL to the output loop:

$$-V_{CC} + I_C R_C + V_{CE} + I_C R_E = 0, \text{ by assuming } R_C = 4.7K\Omega$$

$$\Rightarrow R_E = 1.3K\Omega$$

Apply Thevenin's theorem to the base circuit, then

$$V_{TH} = (V_{CC} R_2) / (R_1 + R_2) \text{ and } R_{TH} = (R_1 R_2) / (R_1 + R_2)$$

We know that the stability factor for a self bias circuit is given by,

$$S = (1 + \beta) / (1 + \beta R_E / (R_{TH} + R_E))$$

$$\Rightarrow R_{TH} = 12.31K\Omega$$

Apply KVL to the input loop, then

$$-V_{TH} + I_B R_{TH} + V_{BE} + I_C R_E = 0$$

$$\Rightarrow V_{TH} = 2.01V$$

Divide R_{TH} with V_{TH}

$$\Rightarrow R_1 = (V_{CC} R_{TH}) / (V_{TH}) = 73.5K\Omega$$

$$\text{Also } R_B = (R_1 R_2) / (R_1 + R_2)$$

$$\Rightarrow R_2 = 14.8K\Omega$$

Design of R_L :-

We know that, gain $A_v = (-h_{fe} R_L^1) / h_{fe}$

$$\Rightarrow R_L^1 = 3K\Omega$$

$$\text{But, } R_L^1 = (R_L R_C) / (R_L + R_C)$$

$$\Rightarrow R_L = 8.3K\Omega$$

Design of C_E and C_{sh} :-

We know that $f_L = (1 + h_{fe}) / 2\pi h_{ie} C_E$

$$\Rightarrow C_E = 100\mu F$$

$$\text{Also } f_H = 1 / 2\pi R_L^1 C_{sh}$$

$$\Rightarrow C_{sh} = 1KPF$$


Assume $C_b = C_C = 10\mu F$ and $R_s = 2.2K\Omega$.

Apparatus:


Sl. No	Name of the component	Specifications or range	Quantity
1	Transistor BC547	$P_d = 500mW$ $I_c(\text{max}) = 100mA$ $\beta = 110-200$	1
2	Capacitor	$10\mu F, 100\mu F, 1KPF$	2,1,1
3	CRO	20MHz	1
4	Resistors	$2.2K\Omega, 74K\Omega,$ $4.7K\Omega, 15K\Omega, 1K\Omega,$ $8.2K\Omega,$	1 each
5	Function generator	1MHz	1
6	Regulated power supply	(0-30)V,1A	1

Theory: Refer Text book to Write Theory related to the experiment.

CircuitDiagram:

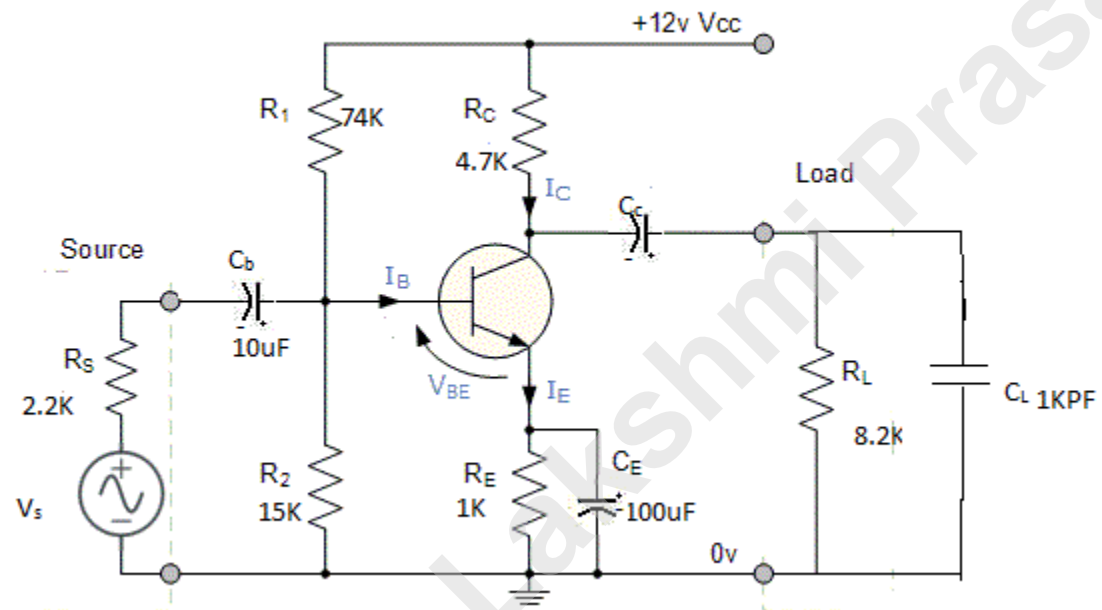

Model Graph:

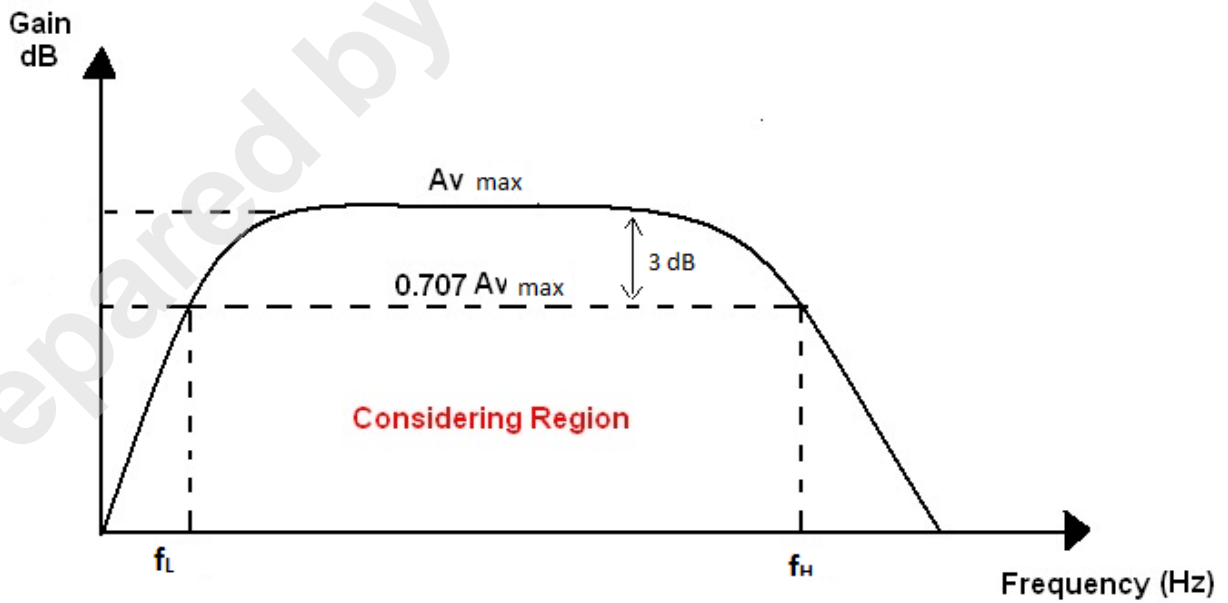

Experimental procedure:

1. Connections are made as per circuit diagram.
2. Apply the input signal of peak to peak amplitude in 30 to 50 mV in range such that the output signal obtained is distortion less.
3. Now change the frequency of the input signal from 50Hz to 500 KHz in suitable steps.
4. Calculate the gain in dB in each step by using the formula $A_v = 20 \log\left(\frac{V_o}{V_s}\right)$.
5. Plot the frequency response of the amplifier by plotting Gain in dB Vs frequency.

Tabular form: input voltage $V_i = \text{-----}$.

Sl. No	Frequency(Hz)	Output voltage(volts)	Gain $\left(\frac{V_o}{V_s}\right)$	Gain in dB $A_v = 20 \log\left(\frac{V_o}{V_s}\right)$.

Precautions:

1. All connections must be done carefully.
2. Switch off power supply before making connections.

Result: Thus the Single Stage RC coupled CE amplifier is designed and its frequency response curve is plotted.

Maximum gain=-----.

Lower cut-off frequency $f_L = \text{-----}$.

Upper cut-off frequency $f_H = \text{-----}$.

Band Width $f_H - f_L = \text{-----}$.