

8.a. Parallel In Parallel Out

Aim: - To develop VHDL code and Test bench code for verification of Parallel In Parallel Out (PIPO) shift register and to perform simulation and synthesis.

Tools required:-Xilinx ISE design software 14.7

Program:-

VHDL code:-

```
library ieee;
use ieee.std_logic_1164.ALL;
entity pipo is Port ( u : in std_logic_vector (5 downto 0);
clk : in std_logic;
rst : in std_logic;
w : out std_logic_vector (5 downto 0));
end pipo;
architecture Behavioral of pipo is
begin
process(u,clk,rst)
begin
if(rst='1')then
w <= "000000";
elsif(clk'event and clk='1')then
w(0) <= u(0);
w(1) <= u(1);
```

```
w(2) <= u(2);
```

```
w(3) <= u(3);
```

```
w(4) <= u(4);
```

```
w(5) <= u(5);
```

```
end if;
```

```
end process;
```

```
end Behavioral;
```

Block Diagram of PIPO:-

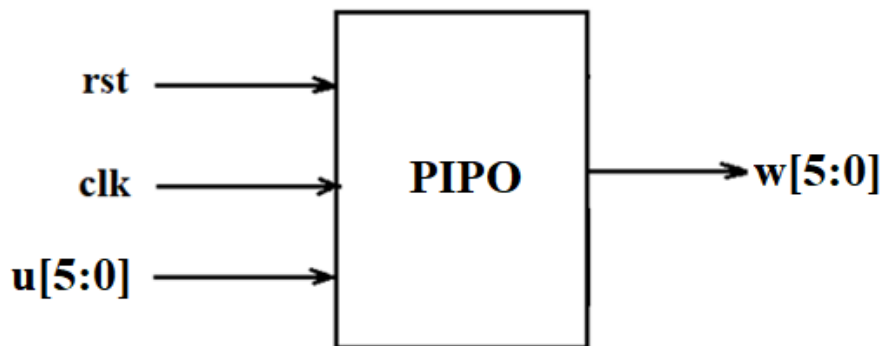


Fig: Parallel In Parallel Out Shift Register

Truth Table of PIPO:-

clk	rst	u[5:0]	W[5:0]
1	0	101101	101101
1	0	111111	111111
1	0	100100	100100
1	1	101110	000000

Device utilization Summary:-


Timing Summary:-

Procedure:-

1. Create a New project.
2. Create a VHDL Module (pipo) ,Write the Logic of the module and save it.
3. In design window right click on VHDL Module and select set as Top module for simulation.
4. Under Implementation select VHDL modules perform synthesize – XST and check syntax for syntax verification.
5. Observe RTL Schematic and Technology schematics.
6. Under Simulation select main module (pipo), perform behavioral check syntax for verification and simulate behavioral model for output waveform.
7. Observe output waveforms by using Force values to rst, clk,u.
8. In Design process Observe Device utilization, Timing summaries.

Result:- The VHDL code and Test bench code for PIPO was developed and verification of synthesis and simulation was performed.

Output waveforms:- PIPO

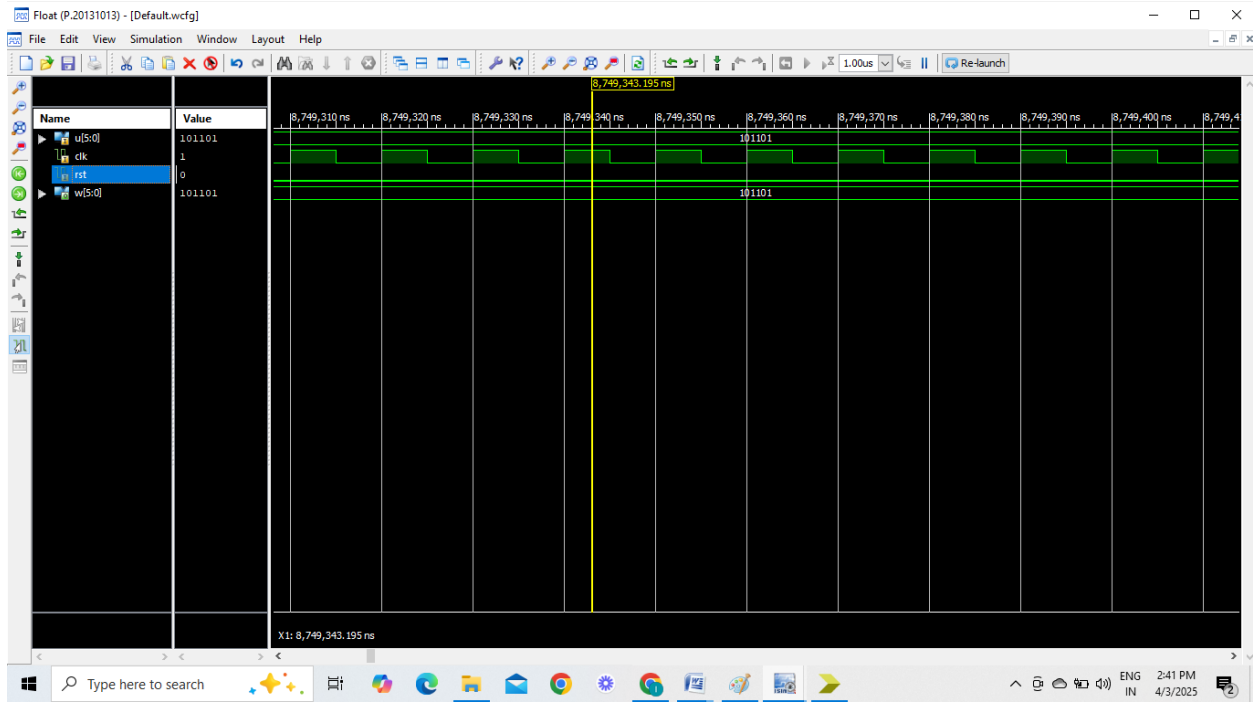

8.b.Serial In Parallel Out

Aim: - To develop VHDL code and Test bench code for verification of Serial In Parallel Out (SIPO) shift register and to perform simulation and synthesis.

Tools required:-Xilinx ISE design software 14.7

Program:-

VHDL code:-

```
library ieee;
use ieee.std_logic_1164.all;

entity sipo is
port(
clk, clear : in std_logic;
Input_Data: in std_logic;
Q: inout std_logic_vector(3 downto 0) );
end sipo;

architecture arch of sipo is
begin
process (clk)
begin
if clear = '1' then
Q <= "0000";
elsif (clk'event and clk='1') then
Q(3 downto 1) <= Q(2 downto 0);
```

```
Q(0) <= Input_Data;
```

```
end if;
```

```
end process;
```

```
end arch;
```

Block Diagram of SIPO:-

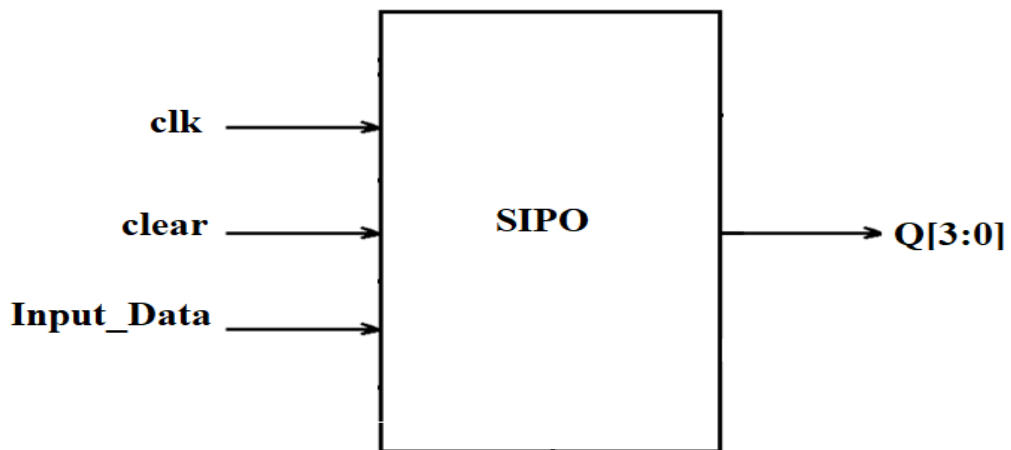


Fig: Serial In Parallel Out Shift Register

Truth Table of SIPO:-

clk	clear	Input_Data	Q[3:0]
1	0	1	1111
1	0	0	0000
1	1	0	0000
1	1	1	0000

Device utilization Summary:-


Timing Summary:-

Procedure:-

1. Create a New project.
2. Create a VHDL Module (sipo) ,Write the Logic of the module and save it.
3. In design window right click on VHDL Module and select set as Top module for simulation.
4. Under Implementation select VHDL modules perform synthesize – XST and check syntax for syntax verification.
5. Observe RTL Schematic and Technology schematics.
6. Under Simulation select main module (sipo), perform behavioral check syntax for verification and simulate behavioral model for output waveform.
7. Observe output waveforms by using Force values to clk,clear,Input_Data.
8. In Design process Observe Device utilization, Timing summaries.

Result:- The VHDL code and Test bench code for SIPO was developed and verification of synthesis and simulation was performed.

Output waveforms:- SIPO

 

8.c.Serial In Serial Out

Aim: - To develop VHDL code and Test bench code for verification of Serial In Serial Out (SISO) shift register and to perform simulation and synthesis.

Tools required:-Xilinx ISE design software 14.7

Program:-

VHDL code:-

```
library ieee;
use ieee.std_logic_1164.all;
entity siso is
port (clk : in std_logic;
rst : in std_logic;
sin : in std_logic;
sout : out std_logic);
end siso;
architecture s1 of siso is
begin
process(clk,rst,sin)
begin
if(rst='1') then
sout <= '0';
elsif(clk='1' and clk'event) then
sout <= sin;
```

```
end if;  
end process;  
end s1;
```

Block Diagram of SISO:-

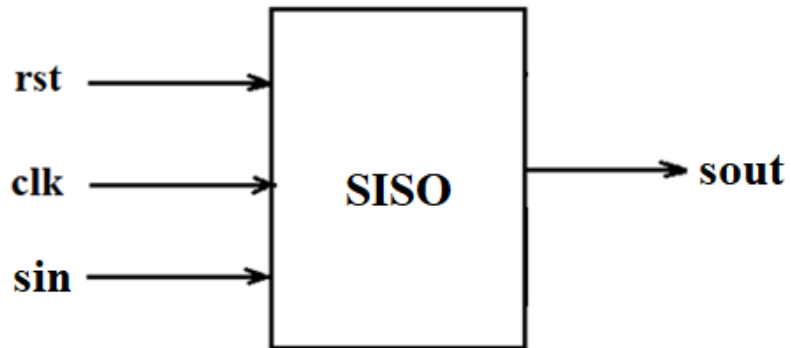


Fig: Serial In Serial Out Shift Register

Truth Table of SISO:-

clk	rst	sin	sout
1	0	0	0
1	0	1	1
1	1	1	0

Device utilization Summary:-

Timing Summary:-

Procedure:-

1. Create a New project.
2. Create a VHDL Module (siso) ,Write the Logic of the module and save it.
3. In design window right click on VHDL Module and select set as Top module for simulation.
4. Under Implementation select VHDL modules perform synthesize – XST and check syntax for syntax verification.
5. Observe RTL Schematic and Technology schematics.
6. Under Simulation select main module (siso), perform behavioral check syntax for verification and simulate behavioral model for output waveform.
7. Observe output waveforms by using Force values to rst, clk,sin.
8. In Design process Observe Device utilization, Timing summaries.

Result:- The VHDL code and Test bench code for SISO was developed and verification of synthesis and simulation was performed.

Output waveforms:- SISO

